

For each circuit:- a) determine the unknown currents and potential differences (show **all** units).
 b) indicate the direction of the current in each branch of the circuit.

